

classmate

Date _____
Page _____

0+0	=	0	0
0+1/1+0	=	1	0
1+1	=	0	1

Unit-4


combinational circuits

combinational circuits

combinational circuits are those digital circuits in which output of the circuit depends ^{only} on the present input. There is no need of feedback in ~~comb~~ and memory in combinational circuits.

eg- half adder, encoder, decoder, subtracter, multiplexer, demultiplexer.

1) HALF ADDER

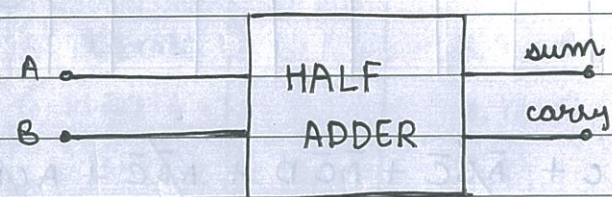

A	B	sum	carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

For sum


A \ B	0	1
0	0	1
1	1	0

$$\Rightarrow \text{sum} = \bar{A}B + A\bar{B}$$

$$\Rightarrow \text{sum} = A \oplus B$$

for carry

A \ B	0	1
0	0	0
1	0	1

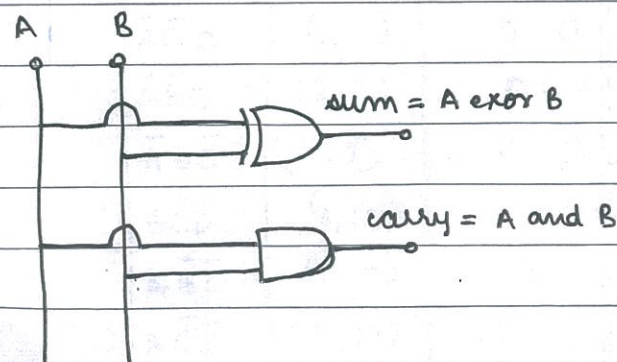

$$\text{carry} = AB$$

$$\text{carry} = A \text{ and } B$$

2) FULL ADDER



A	B	C	sum	carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

for sum

A, B \ C	0	1
00	0	1
01	1	0
11	0	1
10	1	0

for carry

A, B \ C	0	1
00	0	0
01	0	1
11	1	1
10	0	1

$$\text{sum} = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + A\bar{B}C$$

$$\text{sum} = \bar{A}(\bar{B}C + B\bar{C}) + A(\bar{B}\bar{C} + B\bar{C})$$


$$\text{sum} = \bar{A}(B \oplus C) + A(B \oplus C)$$

$$\text{let } (B \oplus C = x, B \oplus C = \bar{x})$$


$$\text{sum} = \bar{A}x + A\bar{x}$$

$$\text{sum} = A \oplus x = A \oplus B \oplus C$$


$$\text{carry} = AC + AB + BC$$

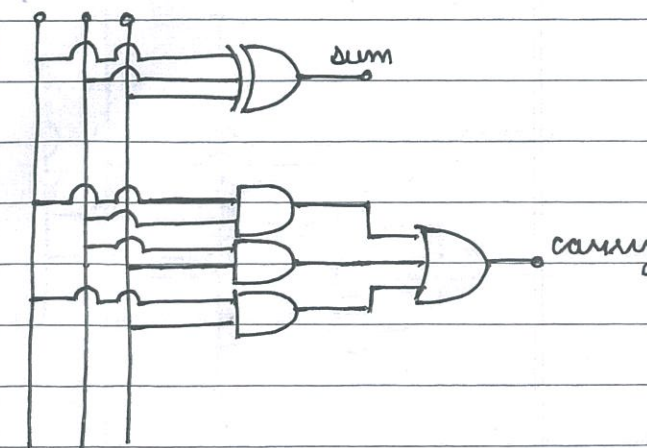


iii) Half Subtractor

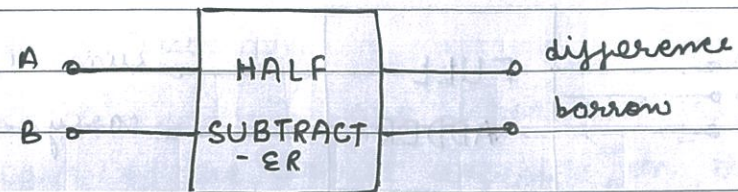


A	B	diff.	borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

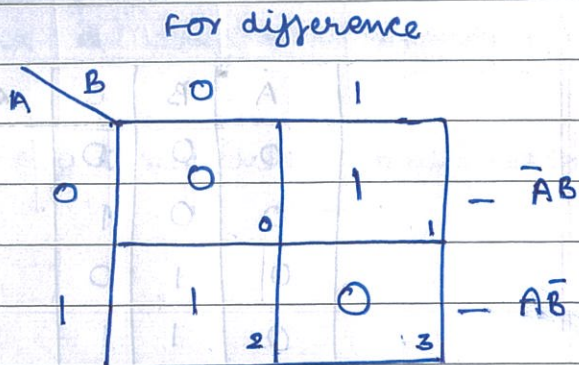


For borrow

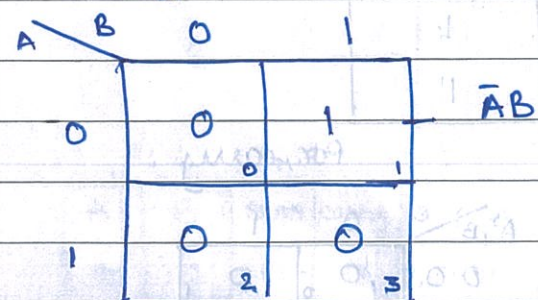

$$\text{Borrow} = \bar{A}B$$

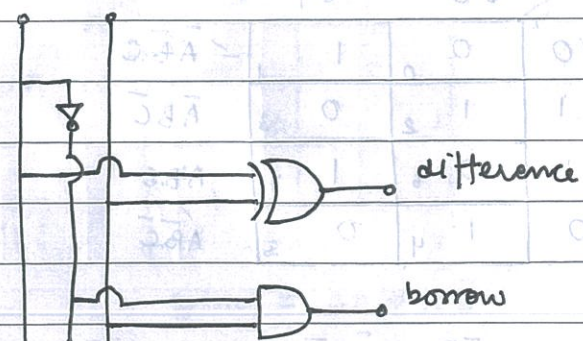

iv) Full Subtractor

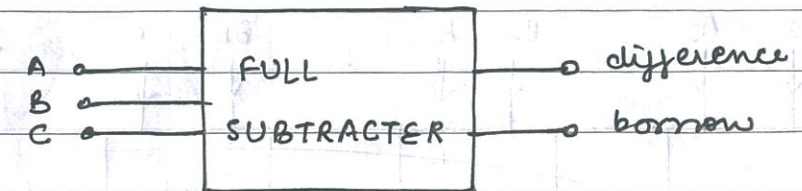

A	B	C	diff.	borrow
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

For difference


A, B \ C	0	1
00	0	1
01	1	0
11	0	1
10	1	0

For borrow

A, B \ C	0	1
00	0	1
01	1	1
11	0	1
10	0	0


$$\begin{aligned} \text{diff} &= \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}C + A\bar{B}\bar{C} \\ &= \bar{A}(\bar{B}C + B\bar{C}) + A(\bar{B}C + \bar{B}\bar{C}) \\ &= \bar{A}(B \oplus C) + A(B \oplus C) \\ &= \text{let } B \oplus C = x \\ &\quad B \oplus C = x \\ \text{diff} &= \bar{A}x + Ax \\ &= A \oplus x \\ &= A \oplus (B \oplus C) \end{aligned}$$
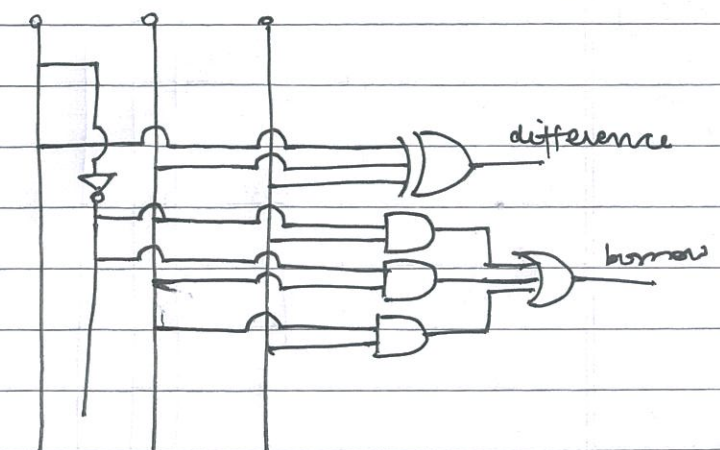
$$\text{borrow} = \bar{A}C + \bar{A}B + BC$$



V) Parallel Adder

4 bit adder

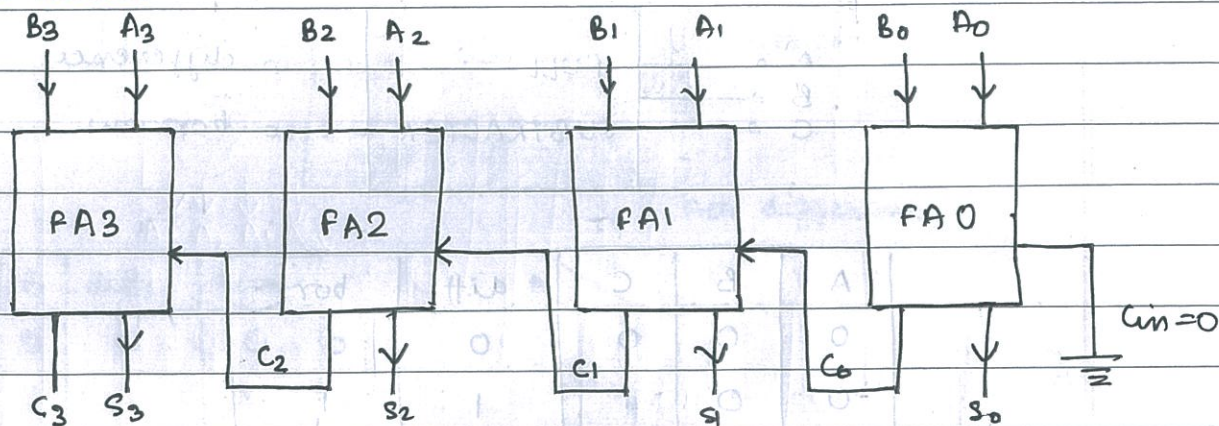

$$\begin{array}{r} 000 \\ A = 1011 \\ B = 1101 \\ \hline S = 1000 \end{array} \quad \begin{array}{c} C_2 \ C_1 \ C_0 \ C_{in}=0 \\ A_3 \ A_2 \ A_1 \ A_0 \\ B_3 \ B_2 \ B_1 \ B_0 \\ S_3 \ S_2 \ S_1 \ S_0 \end{array}$$

i) 4 bit Subtractor


$$A = A_3 \ A_2 \ A_1 \ A_0$$

$$B = B_3 \ B_2 \ B_1 \ B_0$$


$$A - B = (A)_2 + (-B)_2$$


$$= A + (B)_2 \text{'s complement}$$
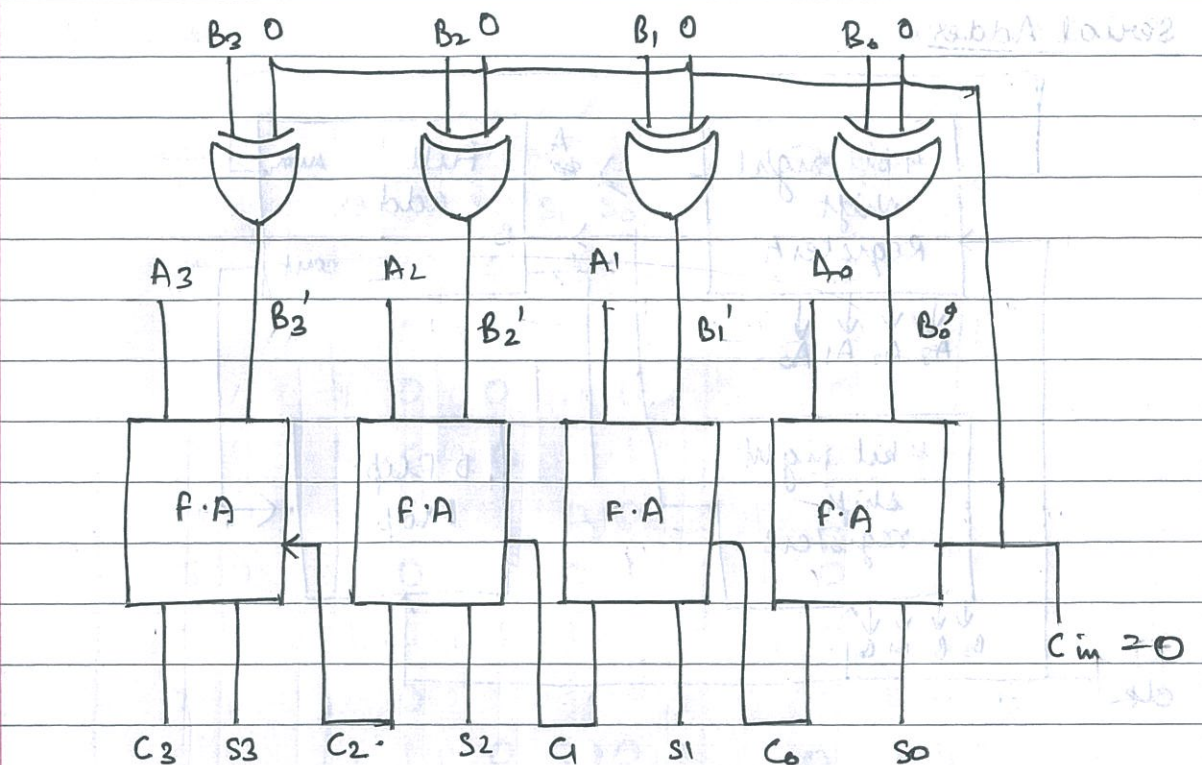
$$(B)_2 \text{'s complement} = B_3' \ B_2' \ B_1' \ B_0'$$



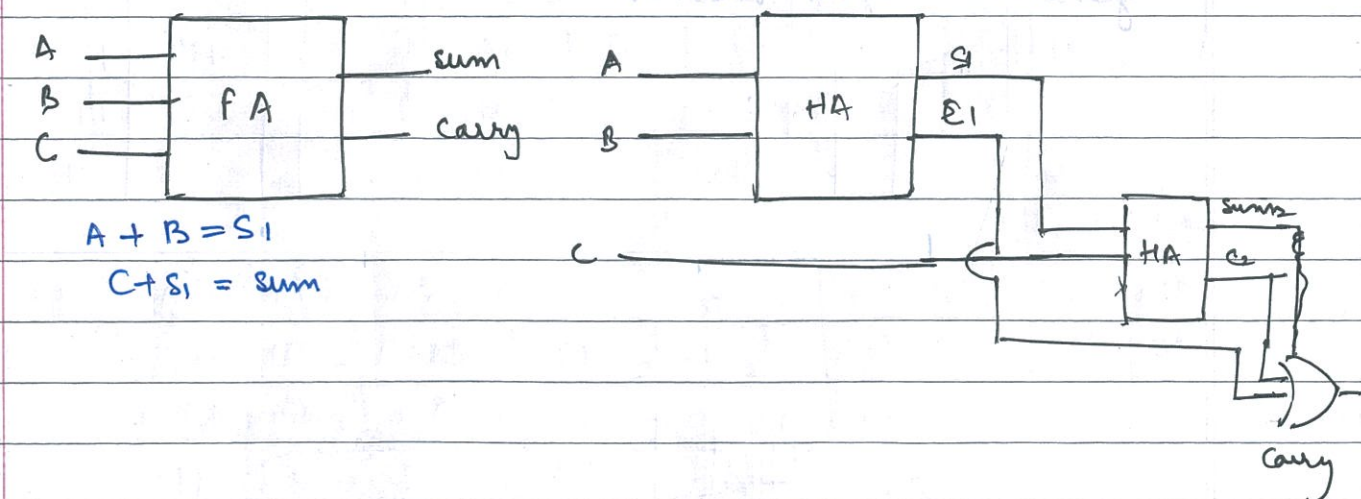Carry over look ahead adder or full adder using Half Adder



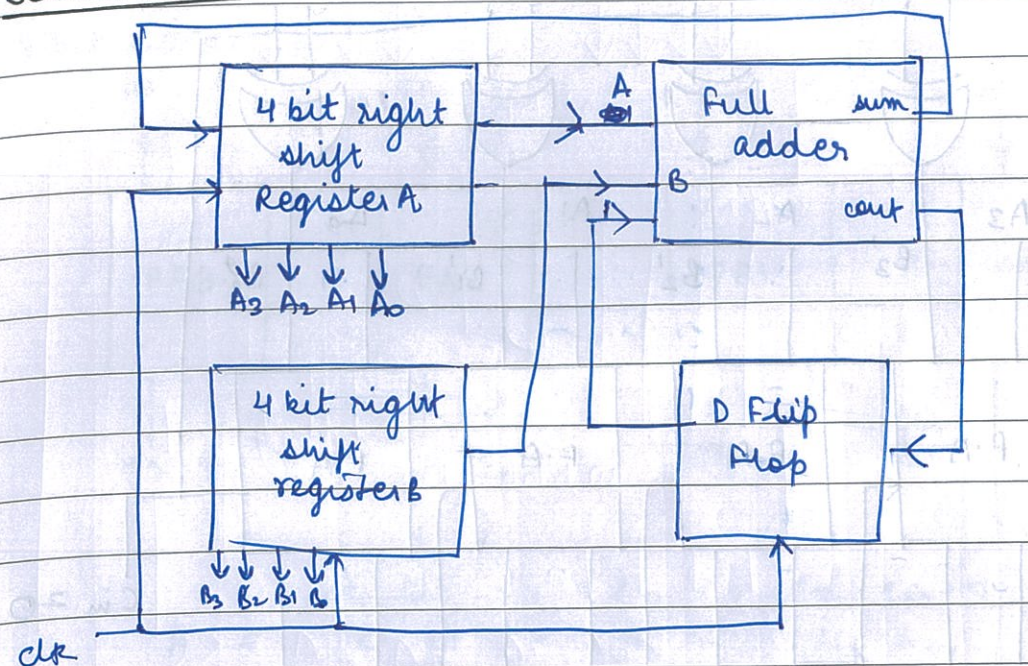Serial Adder


The circuit diagram shows the serial adder. We can add numbers which are stored in a right shift register A and B. The full adder is used to perform bit-by-bit addition and a flip flop is used to store carry output generated after addition.

BCD Adder

Digit	Input				Output Y
	S ₃	S ₂	S ₁	S ₀	
0	0	0	0	0	0
1	0	0	0	1	0
2	0	0	1	0	0
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	0
6	0	1	1	0	0
7	0	1	1	1	0
8	1	0	0	0	0
9	1	0	0	1	0
10	1	0	1	0	1
11	1	0	1	1	1
12	1	1	0	0	1
13	1	1	0	1	1
14	1	1	1	0	1
15	1	1	1	1	1

S ₃ , S ₂	S ₁ , S ₀				S ₃ S ₂	S ₁ S ₀
	00	01	11	10		
00	0 0	0 1	0 2	0 2		
01	0 4	0 5	0 7	0 6		
11	1 12	1 13	1 15	1 14		
10	0 7	0 8	1 10	1 9		

$$Y = S_3S_2 + S_2S_1$$

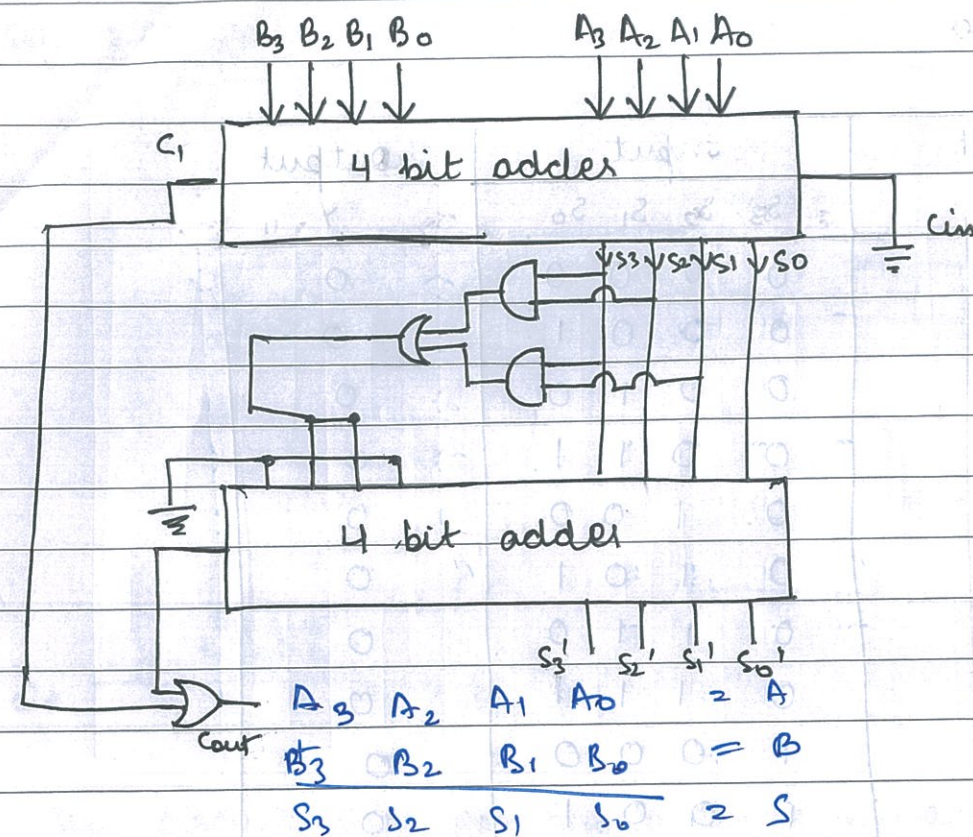

① $S > 9$ $G_{add} = 0110$ $Y = 1$
 $S < 9$ $G_{add} = 0000$ $Y = 0$

B_3, B_2		G_2				B_3, B_2	
		00	01	11	10		
00	00	0	0	0	0	0	2
01	01	1	4	1	5	1	6
11	11	0	12	0	13	0	14
10	10	1	8	1	9	1	10

$G_2 = \bar{B}_3 B_2 + B_2 B_1$
 $= B_2 \text{ xor } B_1$

B_3, B_2		G_1				B_3, B_2	
		00	01	11	10		
00	00	0	0	0	1	0	1
01	01	1	4	1	5	0	6
11	11	1	12	1	13	0	14
10	10	0	8	0	9	1	10

$G_1 = B_2 B_1 + \bar{B}_2 B_1$
 $G_1 = B_2 \text{ xor } B_1$

Binary to Gray Code Converter

Digit	Input				Output			
	B_3	B_2	B_1	B_0	G_3	G_2	G_1	G_0
0	0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0	1
2	0	0	1	0	0	0	1	1
3	0	0	1	1	0	0	1	0
4	0	1	0	0	0	1	1	0
5	0	1	0	1	0	1	1	1
6	0	1	1	0	0	1	0	1
7	0	1	1	1	0	1	0	0
8	1	0	0	0	1	1	0	0
9	1	0	0	1	1	1	0	1
10	1	0	1	0	1	1	1	1
11	1	0	1	1	1	1	1	0
12	1	1	0	0	1	0	1	0
13	1	1	0	1	1	0	1	1
14	1	1	1	0	1	0	0	1
15	1	1	1	1	1	0	0	0

B_3, B_2		G_3				B_3, B_2	
		00	01	11	10		
00	00	0	0	0	0	0	2
01	01	0	0	0	0	0	6
11	11	1	1	1	1	1	14
10	10	1	1	1	1	1	10

$G_3 = B_3$

B_3, B_2		G_0				B_3, B_2	
		00	01	11	10		
00	00	0	0	0	0	0	2
01	01	0	4	1	5	0	6
11	11	0	12	1	13	0	14
10	10	0	8	1	9	0	10

$G_0 = \bar{B}_1 B_0 + B_1 \bar{B}_0$
 $= B_1 \text{ xor } B_0$