

Encoder.


Encoder is a combinational circuit which is designed to perform to convert one number system to another number system format.

Encoder has a 'n' numbers of input lines and 'm' number of output lines.

There are 4 types of encoders.

- i) Octal to Binary encoder.
- ii) Hexa decimal to Binary Encoder.
- iii) Priority Encoder.
- iv) BCD to excess 3 Encoders

Block diagram of Encoder.

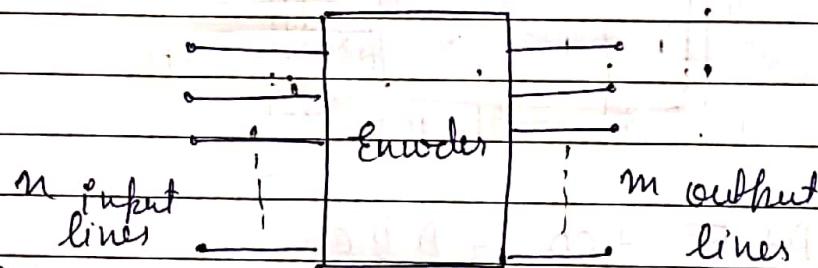

- i) Octal to Binary Encoder.




Digit	D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	B_3	B_2	B_1
0	1	0	0	0	0	0	0	0	0	0	0
1	0	1	0	0	0	0	0	0	0	0	1
2	0	0	1	0	0	0	0	0	0	1	0
3	0	0	0	1	0	0	0	0	0	1	1
4	0	0	0	0	1	0	0	0	1	0	0
5	0	0	0	0	0	1	0	0	1	0	1
6	0	0	0	0	0	0	1	0	1	1	0
7	0	0	0	0	0	0	0	1	1	1	1

Logical Expression.

$$B_0 = D_4 + D_5 + D_6 + D_7$$

$$B_1 = D_2 + D_3 + D_6 + D_7$$

$$B_2 = D_1 + D_3 + D_5 + D_7$$

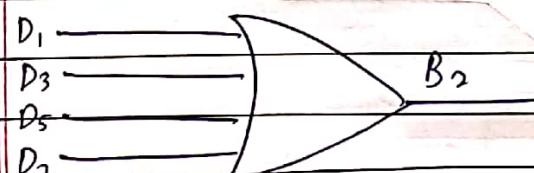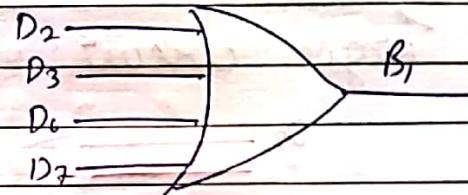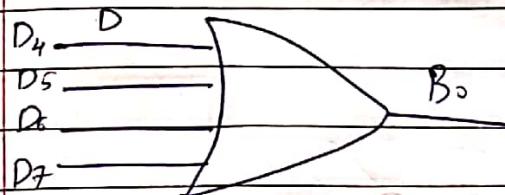

I/P.

O/P

Digits	D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	D_8	D_9	D_{10}	D_{11}	D_{12}	D_{13}	D_{14}	B_{15}	B_0	B_1	B_2
0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
1	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1
2	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1
3	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1
4	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	1	0
5	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	1	0
6	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	1	0
7	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	1	1
8	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0	1	0	0
9	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	1	0	0
10	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	1	0	1
11	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	1	0	1
12	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	1	1	0
13	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	1	1	0
14	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	1	1
15	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	1	1

Logical Expression





$$B_0 = D_8 + D_9 + D_{10} + D_{11} + D_{12} + D_{13} + D_{14} + D_{15}$$

$$B_1 = D_4 + D_5 + D_6 + D_7 + D_{12} + D_{13} + D_{14} + D_{15}$$

$$B_2 = D_2 + D_3 + D_4 + D_5 + D_{10} + D_{11} + D_{14} + D_{15}$$

$$B_3 = D_1 + D_3 + D_5 + D_7 + D_9 + D_{11} + D_{13} + D_{15}$$

Logic circuit

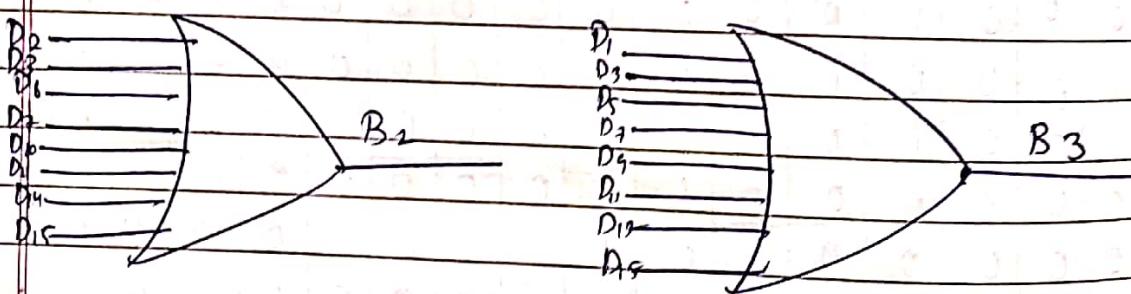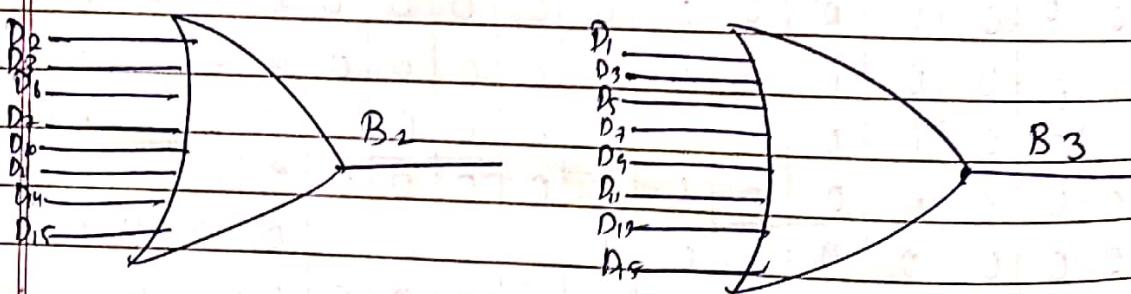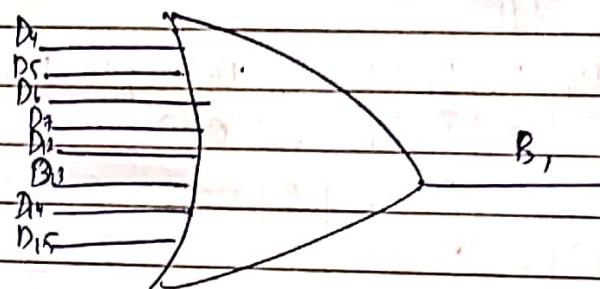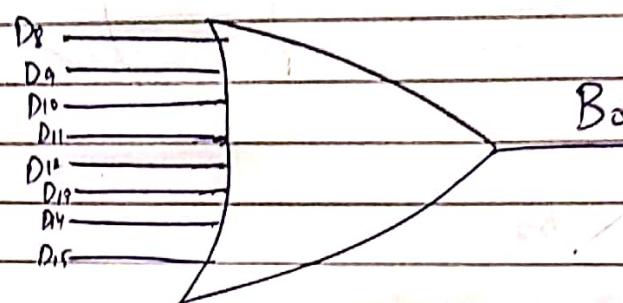


5) a) 19
Decoder

Decoder is a combinational circuit, it convert n - bit binary input into 2^n outputs.

i) 2:4 Decoder.

If Number of bits in input $n=2$

output lines are $2^n = 2^2 = 4$

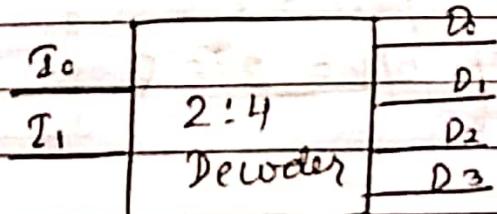


Digit	<u>I/P</u>		<u>O/P</u>			
	I_0	I_1	D_0	D_1	D_2	D_3
0	0	0	1	0	0	0
1	0	1	0	1	0	0
2	1	0	0	0	1	0
3	1	1	0	0	0	1

Logical expression of :-

$$D_0 = \bar{I}_0 \bar{I}_1, \quad D_1 = \bar{I}_0 I_1,$$

$$D_2 = I_0 \bar{I}_1, \quad D_3 = I_0 I_1,$$

Circuit

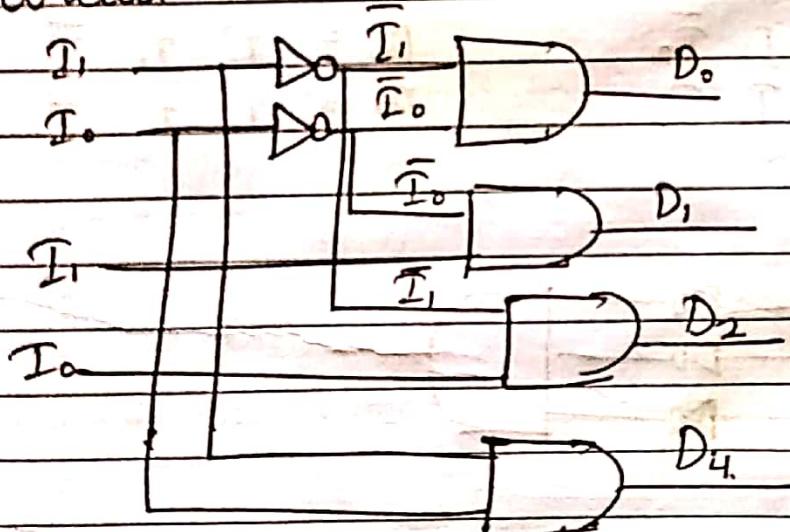


2: 4 Decoder

2) 3:8 Decoder.

If No. of input = 3

$$\text{No. of o/p} = 2^3 = 8$$

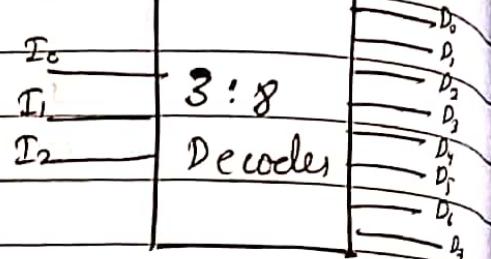

Digits	I ₀	I ₁	I ₂	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
0	0	0	0	1	0	0	0	0	0	0	0
1	0	0	1	0	1	0	0	0	0	0	0
2	0	1	0	0	0	1	0	0	0	0	0
3	0	1	1	0	0	0	1	0	0	0	0
4	1	0	0	0	0	0	0	1	0	0	0
5	1	0	1	0	0	0	0	0	1	0	0
6	1	1	0	0	0	0	0	0	0	1	0
7	1	1	1	0	0	0	0	0	0	0	1

⇒ Logical Expression of

$$D_0 = \bar{I}_0 \bar{I}_1 \bar{I}_2$$

$$D_4 = I_0 \bar{I}_1 \bar{I}_2$$

$$D_1 = \bar{I}_0 \bar{I}_1 I_2$$

$$D_5 = I_0 \bar{I}_1 I_2$$


$$D_2 = I_0 I_1 \bar{I}_2$$

$$D_6 = I_0 I_1 \bar{I}_2$$


$$D_3 = \bar{I}_0 I_1 \bar{I}_2$$

$$D_7 = I_0 I_1 I_2$$

Circuits

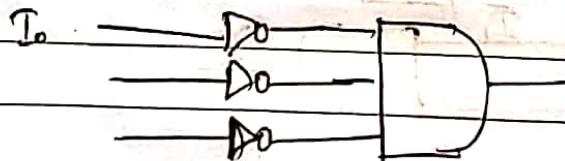

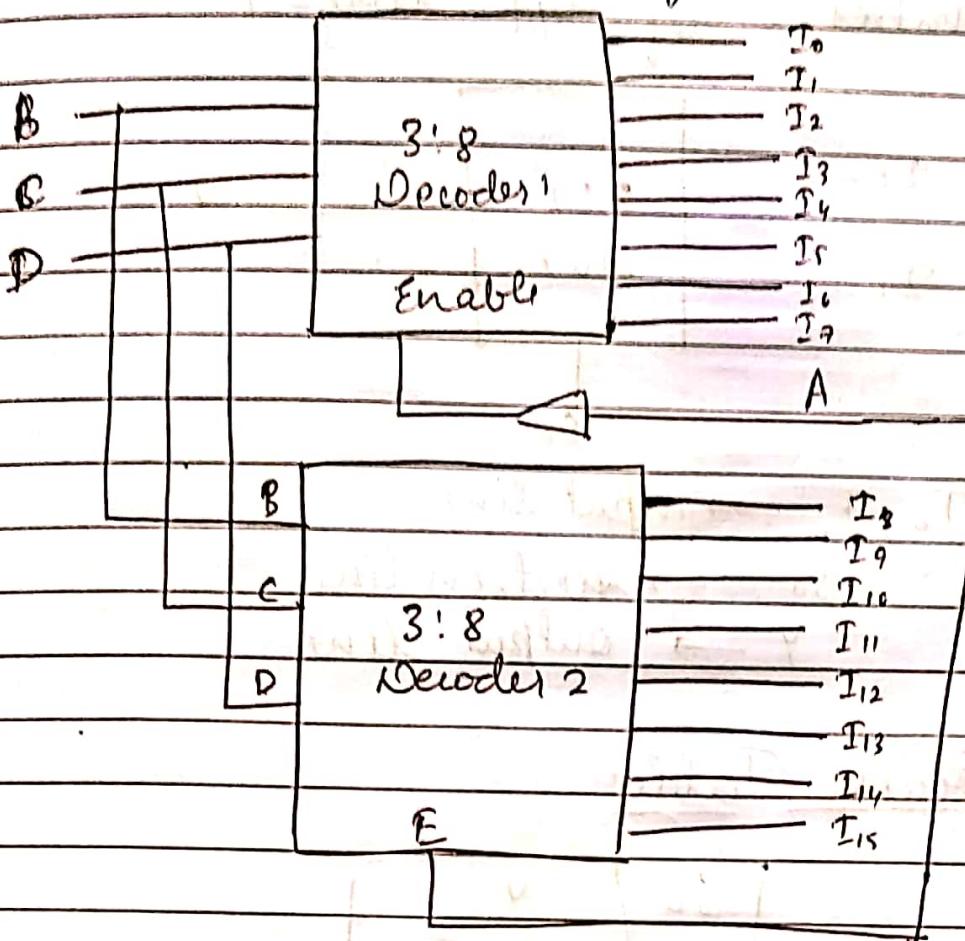Implement 4:16 decoder using 3:8 decoder.



Working

- If $A = 0$, the Decoder 1 is enable & Decoder 2 is disable procedure output to to I_0 to I_7 .
- If $A = 1$, The Decoder 1 is disable & Decoder 2 is enable. Procedure output I_8 & I_{15}


Multiplexer :-

Multiplexer is a special type of combinational circuit it contain n selection lines, 2ⁿ input lines and 1 output line.

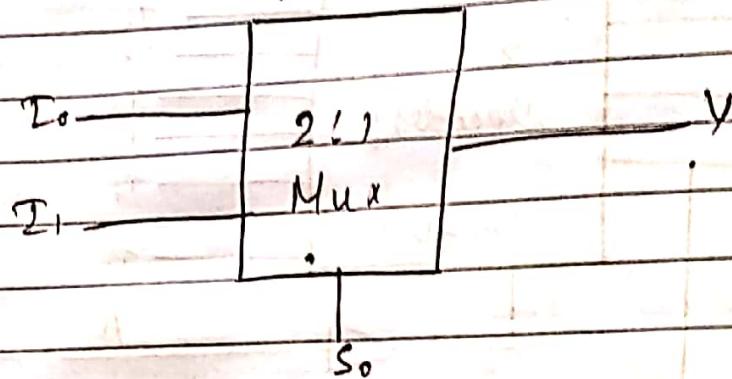2:1 Mux.

Number of i/p lines = $2^1 = 2$.

Number of selection lines = 1
Number of O/P lines = 1



$I_0, I_1 \rightarrow$ input lines.

$S_0 \rightarrow$ selection line

$y \rightarrow$ output line.


Truth Table

S_0	y
0	$y = I_0$
1	$y = I_1$


Logical expression

$$y = \overline{S_0} I_0 + S_0 I_1$$

logical circuit of 2:1 Mux.

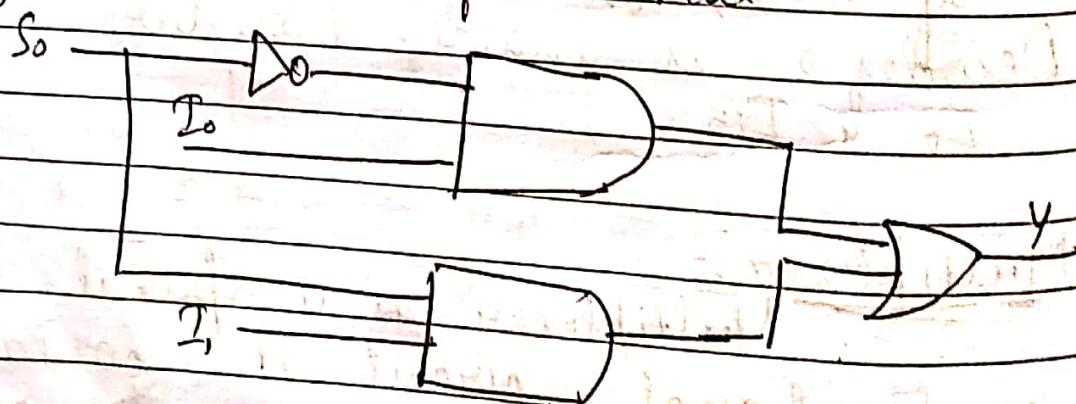

(ii) 4:1 Mux.

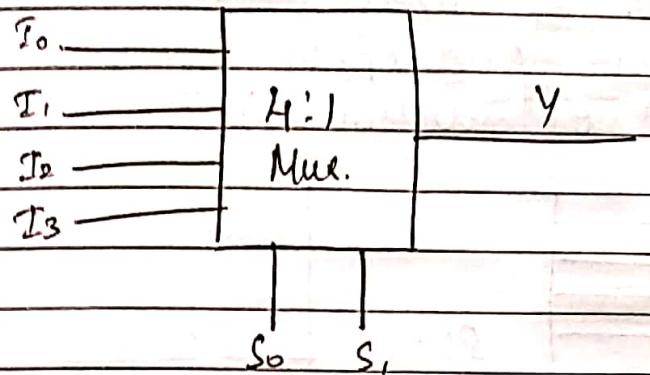Number of i/p lines = $4 = 2^2$

Number of selection lines = 2.

Number of output lines = 1


 T_B

Truth table.

S_0	S_1	Y
0	0	$Y = I_0$
0	1	$Y = I_1$
1	0	$Y = I_2$
1	1	$Y = I_3$

Logical Expression
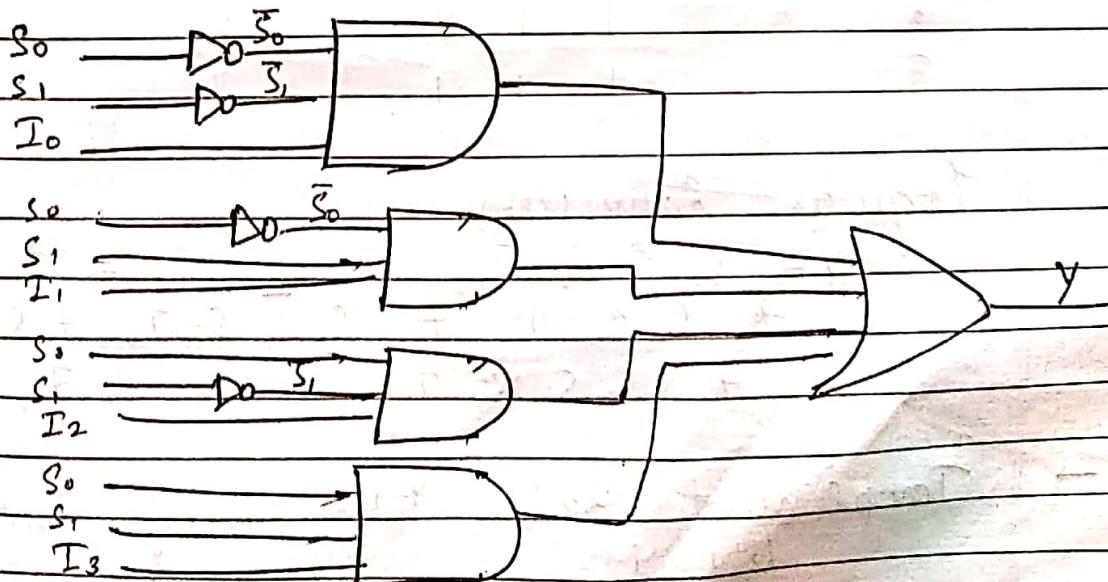
$$Y = \bar{S}_0 \bar{S}_1 I_0 + \bar{S}_0 S_1 I_1 + S_0 \bar{S}_1 I_2 + S_0 S_1 I_3$$




8:1 Mux.

$$\text{Number of Inputs} = 8 = 2^3$$

$$\text{Number of outputs} = 1$$

$$\text{Number of selection lines} = 3$$

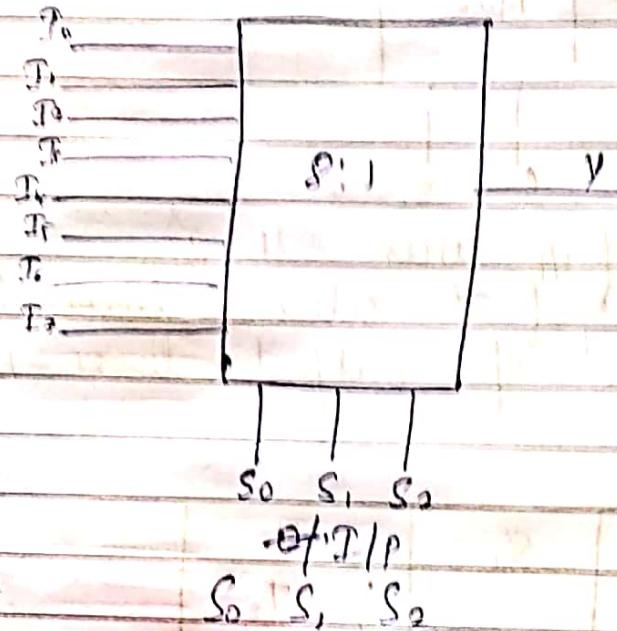

Digit

	$S_0 \quad S_1 \quad S_2$	o/p.
0	0 0 0	$Y = T_0$
1	0 0 1	$Y = T_1$
2	0 1 0	$Y = T_2$
3	0 1 1	$Y = T_3$
4	1 0 0	$Y = T_4$
5	1 0 1	$Y = T_5$
6	1 1 0	$Y = T_6$
7	1 1 1	$Y = T_7$

Logical Expression.

$$Y = \overline{S_0} \overline{S_1} \overline{S_2} \overline{T_0} + \overline{S_0} \overline{S_1} S_2 T_1 + \overline{S_0} S_1 \overline{S_2} T_2 + \\ S_0 \overline{S_1} S_2 T_3 + S_0 \overline{S_1} \overline{S_2} T_4 + S_0 \overline{S_1} S_2 T_5 + \\ S_0 S_1 \overline{S_2} T_6 + S_0 S_1 S_2 T_7$$

⇒ Implement 32:1 Mux using 8:1 and 4:1 Mux.


Implement 32:1 Mux :

Number of I/P = 32.

using 8:1 Mux.

Number of I/P = 8.

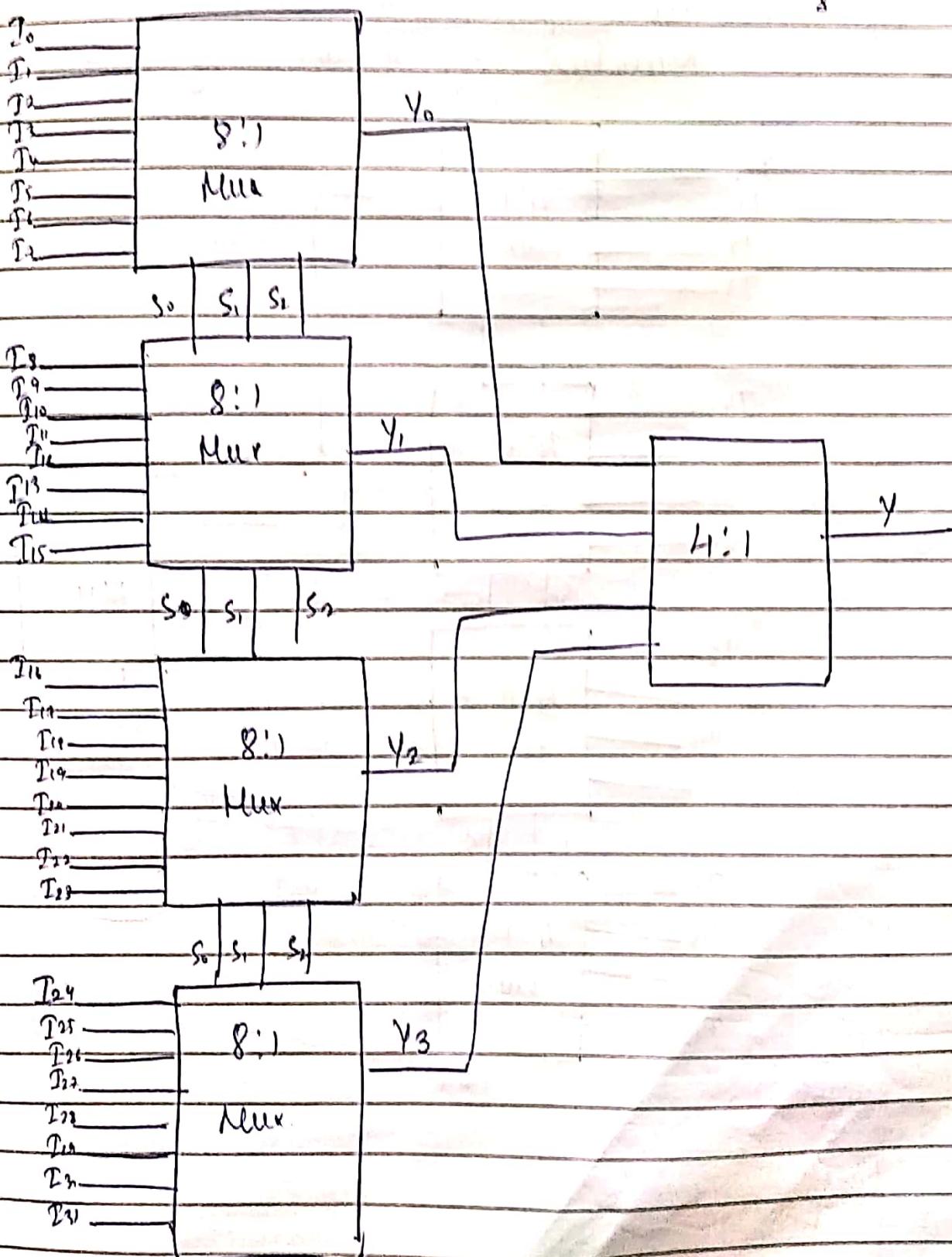Require Number of 8:1 Mux = $\frac{32}{8} = 4$.



→ Implemented 16:1 Mux using 4:1 Mux.


In 16:1 Mux

No. of I/p = 16.

In 4:1 Mux.

No. of I/p = 4.

Number of 4 Mux = $\frac{16}{4} = 4$.

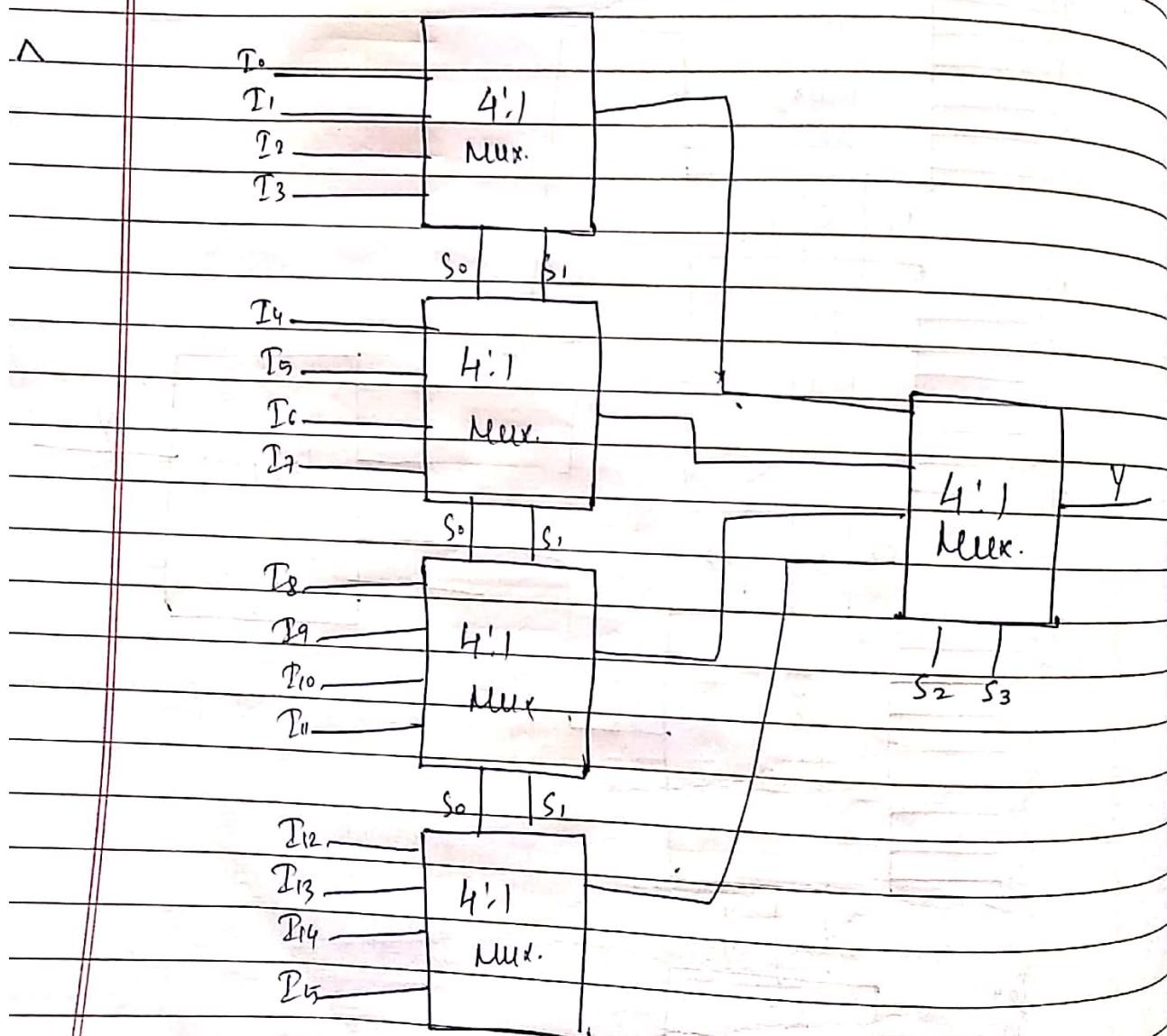

Q) Implement following expression using Mux.


$$f(A, B, C, D) = \sum m(0, 1, 3, 4, 8, 9, 15)$$

Sol: If min term greater than 7, we use 8:1 mux.

	I_0	I_1	I_2	I_3	I_4	I_5	I_6	I_7
\bar{A}	0	1	2	3	4	5	6	7
A	8	9	10	11	12	13	14	15
	1	1	0	\bar{A}	\bar{A}	0	0	A

Note
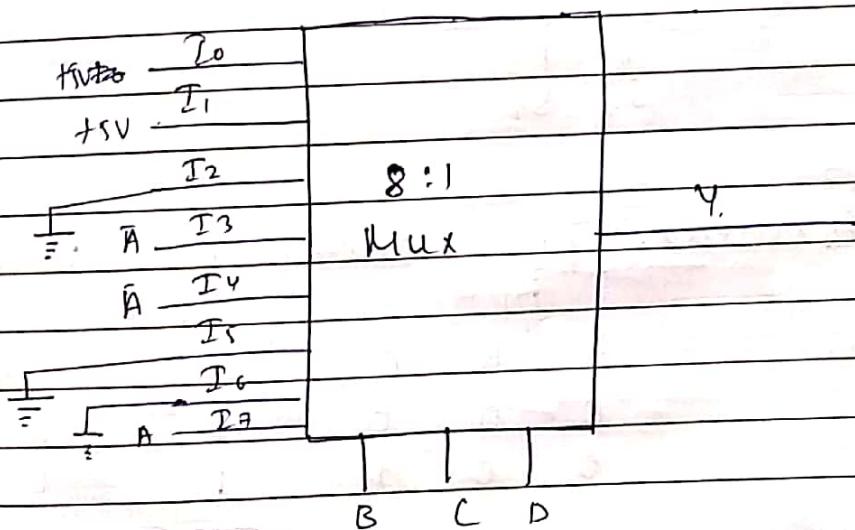
$$\begin{array}{l} \bar{A} \oplus 0 \rightarrow 1, \quad \bar{A} \oplus 1 \rightarrow \bar{A}, \quad \bar{A} \oplus 1 \rightarrow 0 \\ A \oplus 0 \end{array}$$



Q) Implement following logical expression.

i) $y = A\bar{B}\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + ABC$.

Sol:

$$y = A\bar{B}\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + ABC$$

following expression in sop form - [minterm]

$$A\bar{B}C = 101 = 5$$

$$\bar{A}BC = 011 = 3$$

$$A\bar{B}\bar{C} = 110 = 6$$

$$ABC = 111 = 7$$


Value	Mux used
≥ 3	2:1
≥ 7	4:1
≥ 15	8:1

→ selection lines

$$y(A, \bar{B}, \bar{C}) = \Sigma m(3, 5, 6, 7)$$

maximum value is 7 so we use 4:1 mux

	I_0	I_1	I_2	I_3
\bar{A}	0	1	2	3
A	4	5	6	7
	0	A	A	1

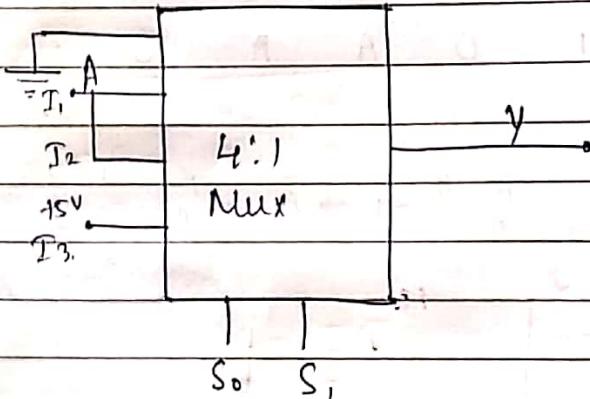

Q: Implement full adder using mux.
i/p o/p

Digit	A	B	C	Sum	Carry.
0	0	0	0	0	0
1	0	0	1	1	0
2	0	1	0	1	0
3	0	1	1	0	1
4	1	0	0	1	0
5	1	0	1	0	1
6	1	1	0	0	1
7	1	1	1	1	1

Value


(min term) is less than 7 so we use 4:1 mux.

$$\text{Sum} = \Sigma m(1, 2, 4, 7)$$




	I_0	I_1	I_2	I_3
\bar{A}	0	1	2	3
A	4	5	6	7

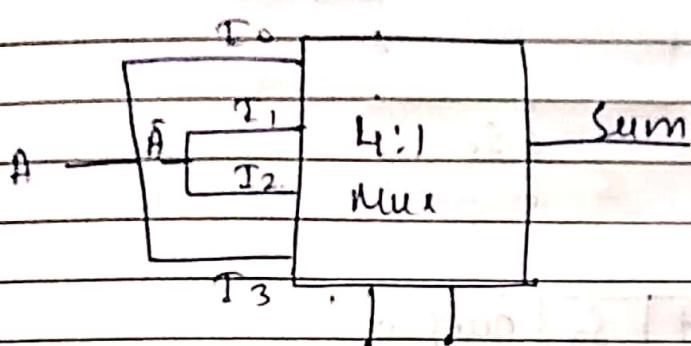$A \quad \bar{A} \quad A \quad \bar{A} \quad A$



$$\text{Carry} = \Sigma.m(3, 5, 6, 7)$$

	I_0	I_1	I_2	I_3
\bar{A}	0	1	2	3
A	4	5	6	7
	0	A	A	1

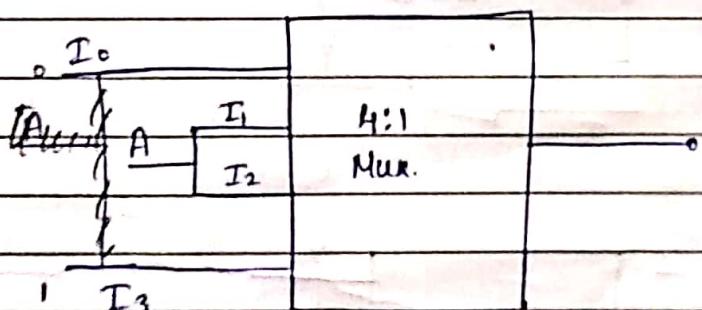


Demultiplexer :- Demultiplexer is a combinational circuit which contain single input, n-selection lines and 2^n output lines.

i) 1:2 Demux

No. of input line = 1

No. of o/p line = $2^1 = 2$

No. of Selection line = 1

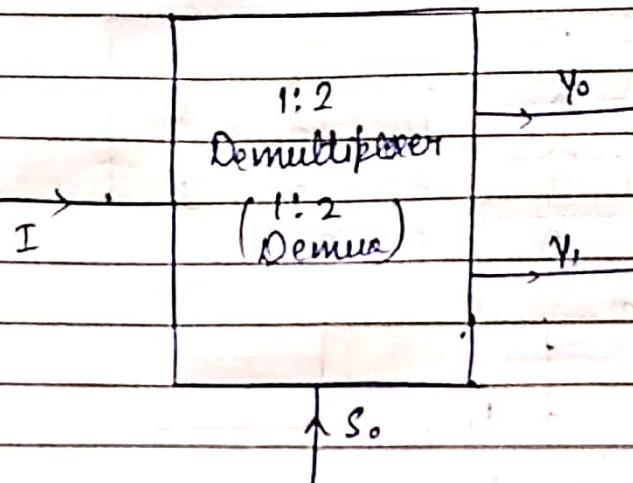Truth table


Digit	S_0	Output
0	0	$Y_0 = I$
1	1	$Y_1 = I$

logical expression


$$Y_0 = IS_0$$

$$Y_1 = IS_0$$

ckt dig :-

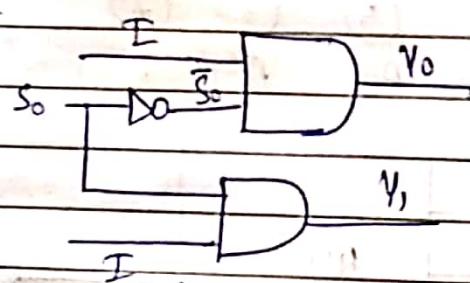

(ii) 1:4 Demux.

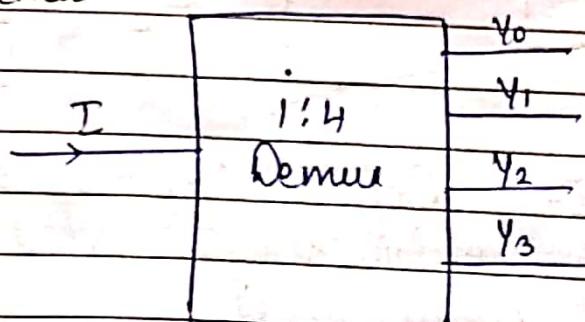

$$\text{No. of ip line} = S_0 + S_1$$

$$\text{No. of o/p lines} = 2^2 = 4$$

$$\text{No. of selection line} = 2$$

Truth Table.


Digit	S_0	S_1	Output
0	0	0	$y_0 = I$
1	0	1	$y_1 = I$
2	1	0	$y_2 = I$
3	1	1	$y_3 = I$

logical expression

$$y_0 = \bar{S}_0 \bar{S}_1, I \quad y_2 = S_0 \bar{S}_1, I$$

$$y_1 = \bar{S}_0 S_1, I \quad y_3 = S_0 S_1, I$$

Ckt dig

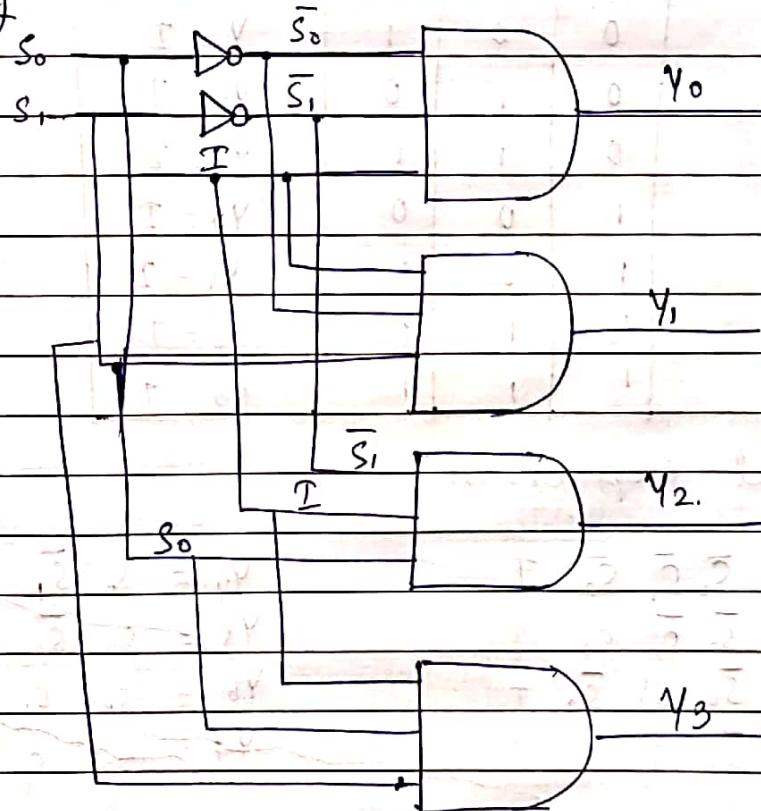


(iii) 1:8 Demux.

$$\text{No. of i/p lines} = 1$$

$$\text{No. of o/p lines} = 2^3 = 8$$

$$\text{No. of Selection line.} = 3$$

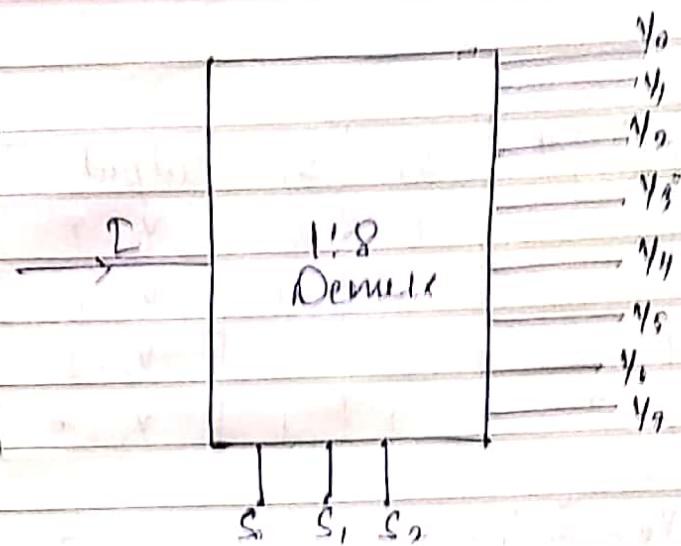

Digit	S_0	S_1	S_2	Y
0	0	0	0	$Y_0 = I$
1	0	0	1	$Y_1 = \bar{I}$
2	0	1	0	$Y_2 = \bar{I}$
3	0	1	1	$Y_3 = \bar{I}$
4	1	0	0	$Y_4 = \bar{I}$
5	1	0	1	$Y_5 = \bar{I}$
6	1	1	0	$Y_6 = \bar{I}$
7	1	1	1	$Y_7 = \bar{I}$

Logical expression:

$$Y_0 = \bar{S}_0 \bar{S}_1 \bar{S}_2 I$$

$$Y_1 = S_0 \bar{S}_1 \bar{S}_2 \bar{I}$$

$$Y_2 = \bar{S}_0 \bar{S}_1 S_2 I$$

$$Y_3 = S_0 \bar{S}_1 \bar{S}_2 \bar{I}$$


$$Y_4 = \bar{S}_0 S_1 \bar{S}_2 I$$




$$Y_5 = S_0 S_1 \bar{S}_2 \bar{I}$$

$$Y_6 = \bar{S}_0 S_1 S_2 \bar{I}$$

$$Y_7 = S_0 S_1 S_2 I$$

Logical ckt:

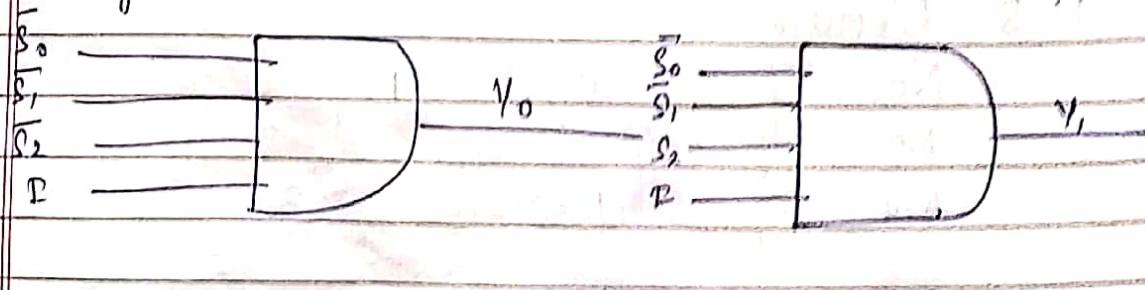

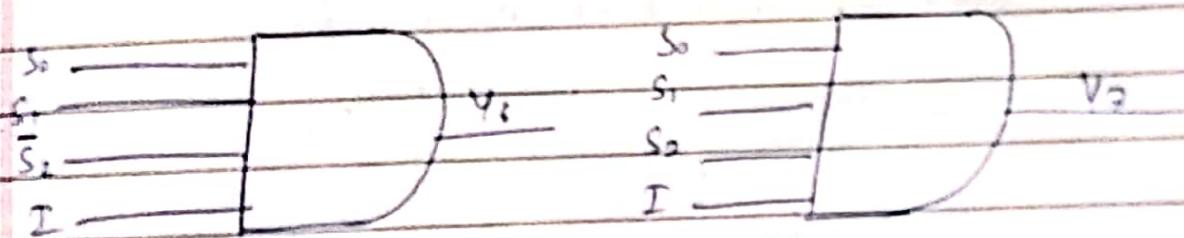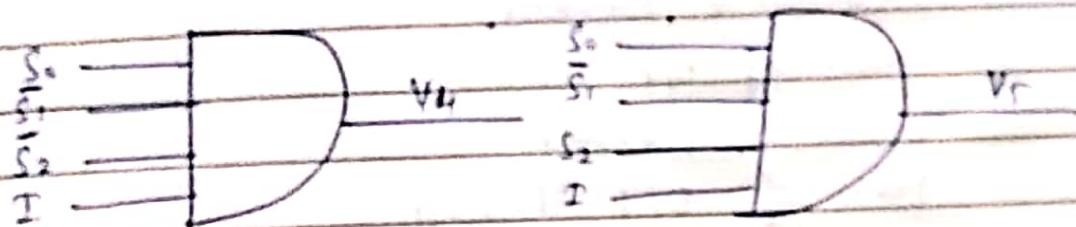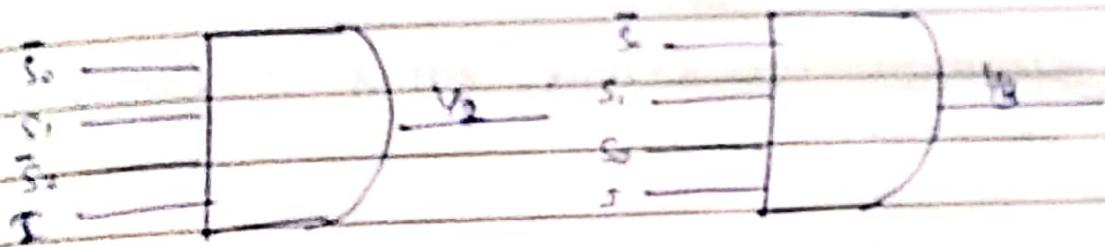

~~3|9|9~~

Q.1 Implement 1:4 Demux using 1:2 Demux.

Ans


In 1:4 Demux.

\Rightarrow No. of O/P line = 4

In 1:2 Demux.

No. of O/P line = 2.

Number of Demux used = $\frac{4}{2} = 2$

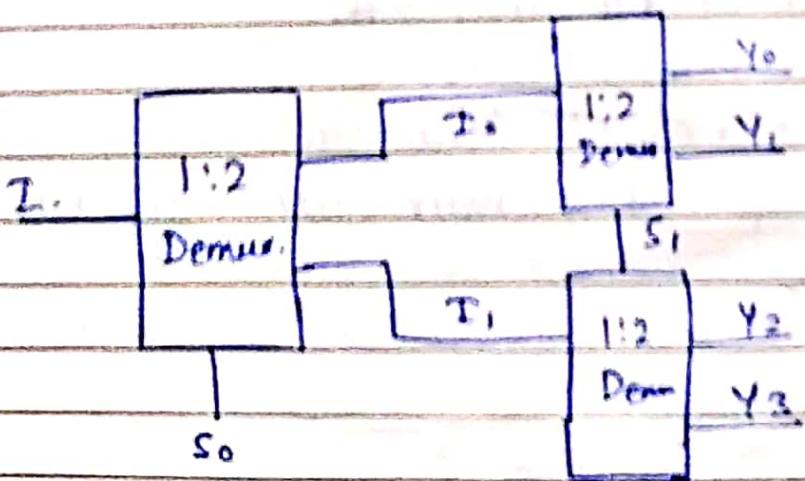

Q.2

Implement 1:8 Demux using 1:4 Demux & 1:2 Demux.

Sol:


In ~~not~~ 1:8 Demux.

No. of o/p line = 8.

In 1:4 Demux.

No. of o/p line = 4.

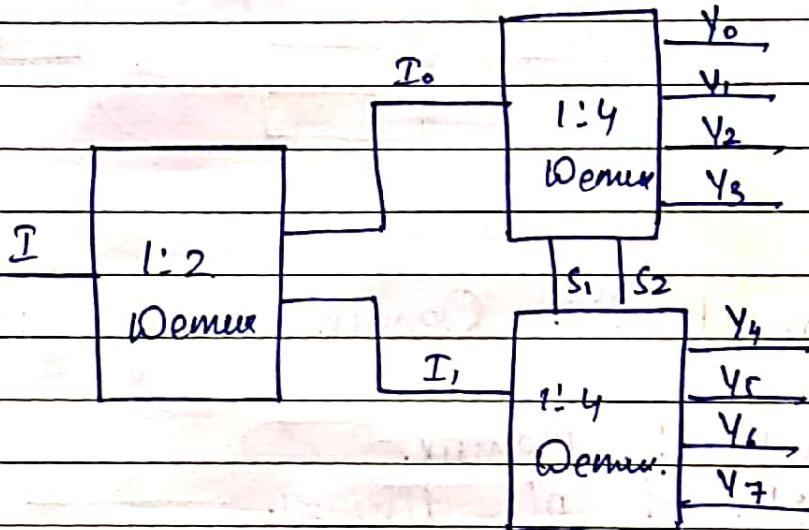No. of 1:4 Demux used = $\frac{8}{4} = 2$



(3)

Implement 1:16 Demux using 1:4 Demux.

Sol:


In 1:16 Demux.

No. of o/p line = 16.

In 1:4 Demux.

No. of o/p line = 4.

No. of 1:4 Demux used = $16 = 4$

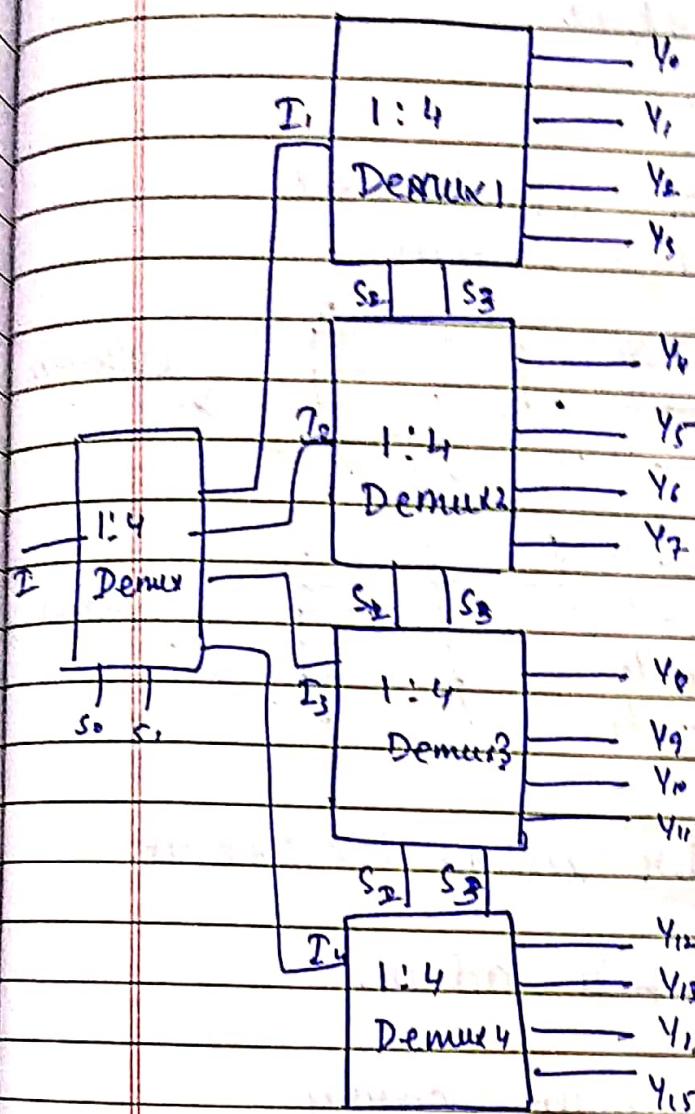

Q.4 Implement full subtractor using 1:8 Demux.

Sol:

Truth table For Full subtractor.

Digit	A	B	C	Difference	Borrow
0	0	0	0	0	0
1	0	0	1	1	1
2	1	0	1	1	1
3	0	1	1	0	1
4	1	0	0	1	0
5	1	0	1	0	0
6	1	1	0	0	0
7	1	1	1	1	1


13/9/19

$$\text{Difference} = \Sigma m(1, 2, 4, 7)$$

$$\text{Borrow} = \Sigma m(1, 2, 3, 7)$$

Maximum value of min term = 7

So we need 1:8 Demux.

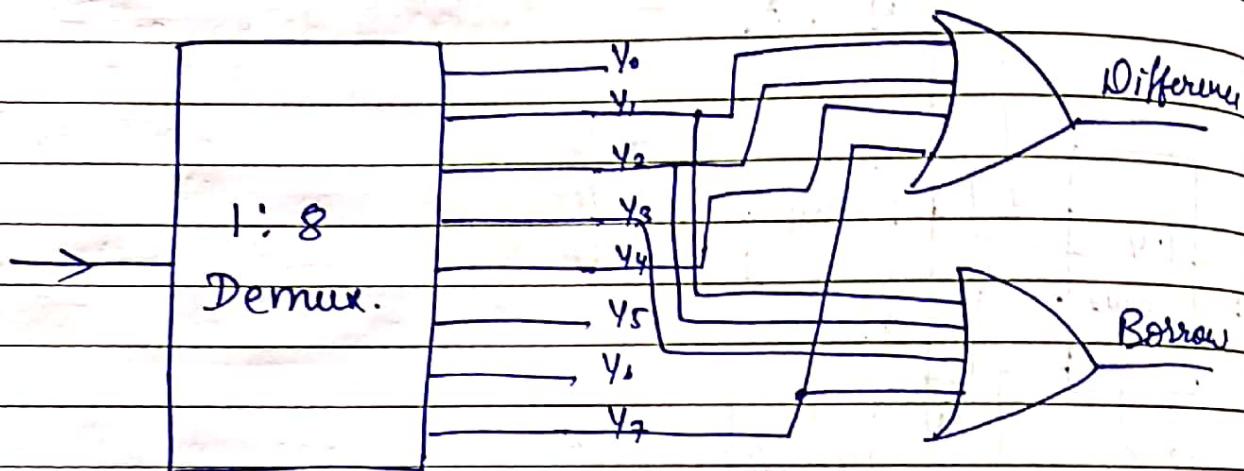

Q.2 Implement full adder using 1:8 Demux.

Solu: Truth table of full adder.

Digit	A	B	C	sum	carry
0	0	0	0	0	0
1	0	0	1	1	0
2	0	1	0	1	0
3	0	1	1	0	1
4	1	0	0	1	0
5	1	0	1	0	1
6	1	1	0	0	1
7	1	1	1	1	1

$$\text{sum} = \Sigma m(1, 2, 4, 7)$$

$$\text{carry} = \Sigma m(3, 5, 6, 7)$$

30/9/19

Code Converter:-

Binary to Grey code converter.

Ex-03

Digit	Input				Output				$0 \oplus 0 = 0$ $0 \oplus 1 = 1$ $1 \oplus 0 = 1$ $1 \oplus 1 = 0$
	B_3	B_2	B_1	B_0	G_3	G_2	G_1	G_0	
0	0	0	0	0	0	0	0	0	
1	0	0	0	1	0	0	0	1	
2	0	0	1	0	0	0	1	1	
3	0	0	1	1	0	0	1	0	
4	0	1	0	0	0	1	1	0	
5	0	1	0	1	0	1	1	1	
6	0	1	1	0	0	1	0	1	
7	0	1	1	1	0	1	0	0	
8	1	0	0	0	1	1	0	0	
9	1	0	0	1	1	1	0	1	
10	1	0	1	0	1	1	1	1	
11	1	0	1	1	1	1	1	0	
12	1	1	0	0	1	0	1	0	
13	1	1	0	1	1	0	1	1	
14	1	1	1	0	1	0	0	1	
15	1	1	1	1	1	0	0	0	

K Map for G_3

$B_3\backslash B_2$	00	01	011	10
00	0	0	0	0
01	0	1	3	2
011	4	5	7	6
10	11	13	15	14
	1	1	1	1
	10	8	9	11
				10

$$G_3 = B_3$$

K Map for G_2

B_3, B_2	00	01	11	10	
00	0, 0	0, 1	0, 3	0, 2	
01	1, 4	1, 5	1, 7	1, 6	$\rightarrow \bar{B}_3 B_2$
11	0, 12	0, 11	0, 15	0, 14	
10	1, 8	1, 9	1, 11	1, 10	$\rightarrow B_3 \bar{B}_2$

$$G_2 = \bar{B}_3 B_2 + B_3 \bar{B}_2 \\ = B_3 \text{ XOR } B_2.$$

K Map for G_1

B_3, B_2	00	01	11	10	
00	0, 0	0, 1	1, 3	1, 2	
01	1, 4	1, 5	0, 7	0, 6	
11	1, 12	1, 13	0, 6	0, 15	
10	0, 8	0, 9	1, 11	1, 10	$\rightarrow B_2 B_1$

$$G_1 = \bar{B}_2 B_1 + B_2 \bar{B}_1$$

$$G_1 = B_2 \text{ XOR } B_1$$


K Map for G_0

B_3, B_2	00	01	11	10	
00	0, 0	1, 0	0, 3	1, 2	$\rightarrow \bar{B}_1 B_0$
01	0, 4	1, 5	0, 7	1, 6	
11	0, 12	1, 13	0, 15	1, 14	
10	0, 8	1, 9	0, 11	1, 10	

$$G_0 = \bar{B}_1 B_0 + B_1 \bar{B}_0$$

$$G_0 = B_1 \text{ XOR } B_0$$

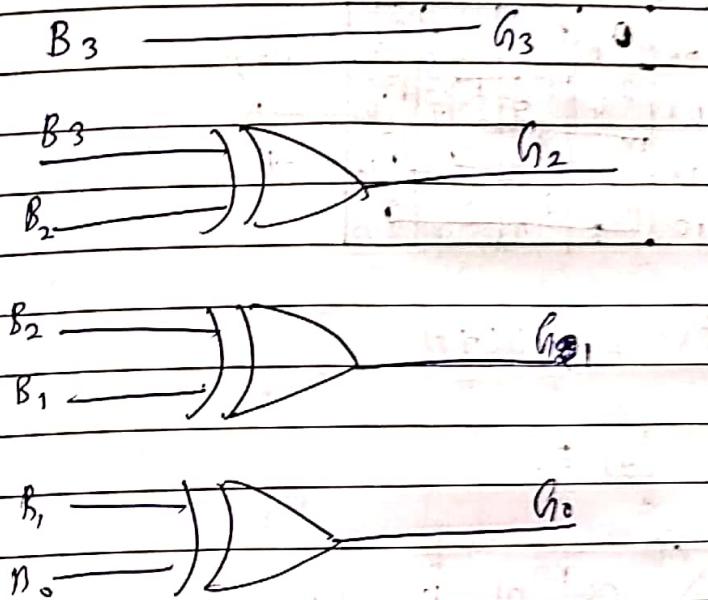Logical circuit For Binary to Gray code converter.



(ii) BCD to Excess 3 code converter.

Digit	Input				Output			
	A	B	C	D	E ₃	E ₂	E ₁	E ₀
0	0	0	0	0	0	0	1	1
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	0	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	1	1
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	0	1
7	0	1	1	1	1	0	1	0
8	1	1	0	0	1	0	1	1
9	1	1	0	1	1	1	0	0
10	1	0	1	0	x	x	x	x
11	1	0	1	1	x	x	x	x
12	1	1	0	0	x	x	x	y
13	1	1	0	1	x	x	x	x
14	1	1	1	0	x	x	x	x

(i) K Map for F_3

		C, D.				
		00	01	11	10	
A, B		00	0	0	1	0
00		01	0	1	1	1
01		11	X	X	X	X
11		10	1	1	X	X

 BD BC A

$$F_3 = BD + BC + A$$

(ii) K Map for F_2

		CD				
		00	01	11	10	
A, B		00	0	0	1	1
00		01	1	0	1	1
01		11	X	X	X	X
11		10	0	1	X	X

 $\bar{A}\bar{B}C$ AD $\bar{B}D$

$$F_2 = AD + \bar{B}D + \bar{A}\bar{B}C + B\bar{C}\bar{D}$$

K Map for F_1

		CP				
		00	01	11	10	
AB		00	1	0	1	1
00		01	1	0	1	0
01		11	X	X	X	X
11		10	1	0	X	X

$$F_1 = \bar{C}\bar{D} + C\bar{D}$$

= CEXNOR

K Map for F_0

		CP				
		00	01	11	10	
AB		00	1	0	1	0
00		01	1	0	1	0
01		11	X	X	X	X
11		10	1	0	X	X

$$F_0 = \bar{P}$$

